


# RGB led strip driver

Wemos D1 mini V2



RGB led strip driver shield

This one is an Open-Smart (P9813 chip)


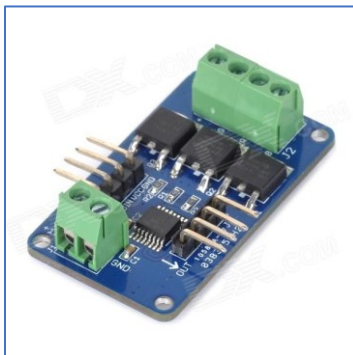


Mini DC-DC 12-24 V Naar 5 V 3A Step Down Voedingsmodule Buck Converter

Before use trim the output voltage to 5 volt.



How to connect

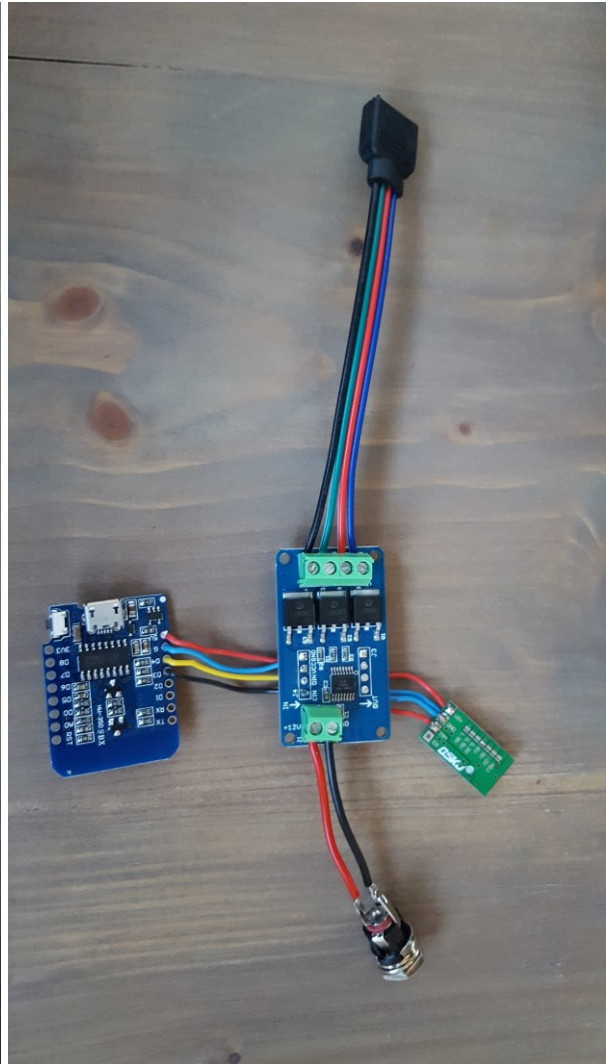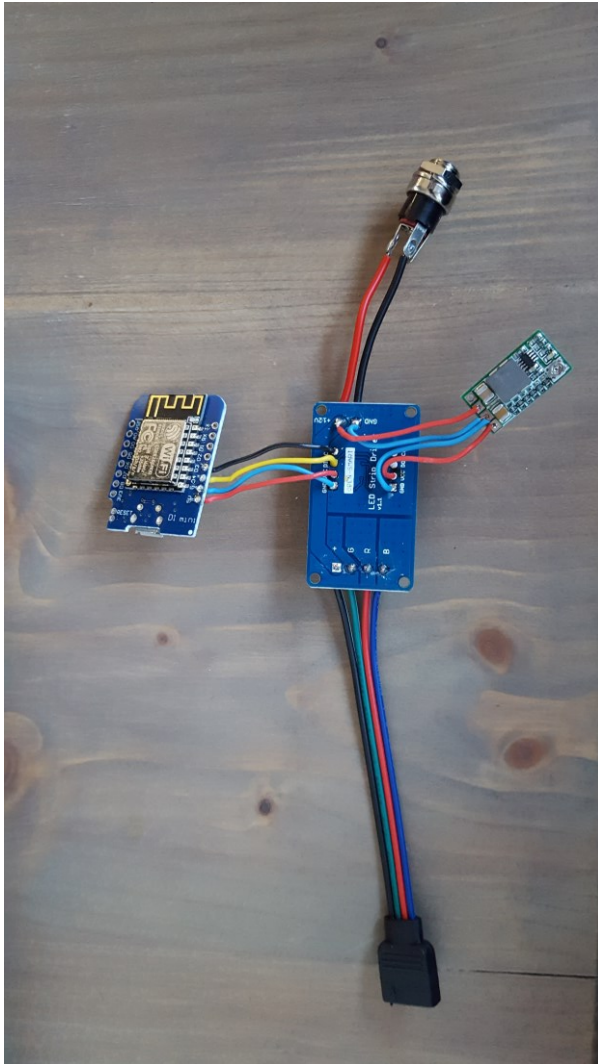

Put it into the box

<https://www.tinkercad.com/things/8Ej6zM3998g-homeyduino-rgb-driver-box>

